

# **Ultra-Low Power PLL for Wake-up Receiver Applications**

## **Specialization Project Progress - 6th Week**

Cole Nielsen

Department of Electronic Systems, NTNU

4 October 2019 (Calendar week 40)

# Autumn Timeline

Week	Dates	Tasks	Outcomes
36	2.9 - 8.9	Review PLL Design	Refreshed Knowledge
37	9.9 - 15.9	Modeling/simulation (set up)	–
38	16.9 - 22.9	Modeling/simulation	TDC/DCO Requirements
39	23.9 - 29.9	Modeling/simulation	Loop Filter/Digital Algorithms
40	30.9 - 6.10	Modeling/simulation	Loop filter, DCO, TDC, calibration
41	7.10 - 13.10	Circuit Research	DCO/Divider topologies, Ideal Virtuoso implementation
42	14.10 - 20.10	Circuit Research	TDC/other topologies
43	21.10 - 27.10	Circuit Implementation	Digital logic (schematic)
44	28.10 - 3.11	Circuit Implementation	DCO (schematic)
45	4.11 - 10.11	Circuit Implementation	Divider/other (schematic)
46	11.11 - 17.11	Circuit Implementation (TDC)	
47	18.11 - 24.11	Circuit Implementation (TDC)	TDC (schematic)
48	25.11 - 1.12	Full Circuit testing	Testbenches, find bugs, design fixes
49	2.12 - 8.12	Full Circuit testing	Design Fixes/iteration
50	9.12 - 15.12	–	–

Legend: Done Current Revised

# Timeline Tasks


## This week

- Originally planned on implementing ideal simulation in Virtuoso using ideal library components and some Verilog.
- *What I actually did:*
  - Found issue with how I defined phase noise requirements
    - Had to redefine this, the TDC and loop bandwidth specification.
  - Had to rework DCO simulation model to have accurate phase noise.
  - Analyzed sensitivity/variation of DCO gain for loop filter analysis.
  - Analyzed TDC to determine accuracy/linearity (tied to calibration)
  - Decided to change loop filter to use PI-based control.

# Requirements redefinition
 
## Redefining phase noise and loop bandwidth requirements

- *Made bad assumption with original requirements*, i.e. residual frequency modulation is predicated on a Gaussian phase noise distribution.
- Now redefined in terms of the actual spectrum of the PLL for use with 2FSK. Phase noise is derived from the closed loop PLL transfer function  $G(f)$ .
- Bandwidth is now selected to minimize amount of power that overlaps in 2FSK tones.
  - (Integrated PSD in overlap)/(total power) = bit error probability.



# Requirements redefinition

## Loop definition and phase noise components.

- Phase noise and closed loop response  $G(f)$  are simple to define. Second order butterworth  $G(f)$  is desired. Loop bandwidth =  $\omega_N$ ,  $\zeta = 0.707$ :



$$G(f) = \frac{\omega_N^2}{s^2 + 2\zeta\omega_N s + \omega_N^2} \quad (1)$$

- The TDC quantization phase noise is given by:

$$PN_{TDC}(f) = f_{ref} \cdot |2\pi N G(f)|^2 \cdot \frac{\Delta t_{del}^2}{12} \quad (2)$$

- The oscillator phase noise (based on ring oscillator theoretical limit) is:

$$PN_{osc}(f) = |1 - G(f)|^2 \cdot \frac{7.33k_B T}{P_{osc}} \cdot \left(\frac{f_0}{f}\right)^2 \quad (3)$$

  

# Requirements redefinition

## Connecting BER, loop bandwidth, frequency deviation.

- Need to calculate power of oscillator within  $\Delta f$  of the carrier. If  $V_{osc} = \Re(e^{j\omega_0 t - j\phi_{noise}(t)})$ , and  $\phi_{noise}(t)$  is small:

$$\Re(e^{j\omega_0 t - j\phi_{noise}(t)}) \approx \Re(e^{j\omega_0 t}(1 - j\phi_{noise}(t))) = \cos(\omega_0 t) + \phi_{noise}(t) \sin(\omega_0 t) \quad (4)$$

- The power within  $\Delta f$  of the carrier is (if the carrier is normalized to a power of 1):

$$P_{out}(\Delta f) = 1 + 2 \int_0^{\Delta f} \phi_{noise}^2(t) df \quad (5)$$




- To find the minimum FSK frequency deviation for a given BER, the following is solved computationally. This is based on the overlap principle. ( $f_{dev} = \Delta f$ )

$$P_{out}(\Delta f = \infty) \cdot (1 - 2BER) = 1 + 2 \int_0^{f_{dev}} \phi_{noise}^2(t) df \quad (6)$$

# Requirements redefinition
   
## Solving for loop bandwidth computationally

- Most power from phase noise is accumulated near frequency of loop bandwidth.
- TDC and DCO noise were optimized to provide approximately the same contribution to phase noise.
- For 250 kHz of frequency deviation,  $\leq 70$  kHz of closed loop bandwidth is required.
- Selecting 50 kHz loop bandwidth, with 64 TDC steps to allow for 50 kHz margin on BER=1e-2 with  $f_{dev} = 250$  kHz.



# Loop Filter

## Resolving unknowns

- Thoughtful loop filter design requires consideration of some physical parameters
  - **TDC accuracy**
    - Affects PLL transfer function, so we want to minimize variation.
    - Innately tied to calibration process.
    - Important for accurate calibration of frequency, to hit PLL lock-in range.
    - Important for INL; also DNL associated with TDC phase wrap-over.
  - **$K_{DCO}$  and variance of  $K_{DCO}$** 
    - Very important in determining gain coefficients in loop filter.
    - Variance of  $K_{DCO}$  will be **the most** significant factor in overall PLL loop performance variation, and will be hard to calibrate.
    -
- Consequently, I analyzed the real-hardware considerations for these parameters to provide some inside into the loop design.



# TDC accuracy


## Resolving unknowns

- Had to look into TDC circuit architectures to consider question accuracy and calibration.
- **Analog or digital??**
  - **Analog**
    - (+) Better accuracy (always running)?
    - (-) Constant Power draw from CP/loop filter
    - (-) Have to wait for lock everytime
  - **Digital**
    - Calibrate once, run for a long time before recalibrating.
    - Lower overall power.
    - Inherent drift.
    - Possibility - Counter based design requiring no calibration???
- Currently believe digital will have power supremacy.
- Targeting  $\pm 50$  ppm accuracy to correspond to  $\pm 120$  kHz at 2.4 GHz.

# Analog TDC

 
## Traditional Analog DLL

- Simple analog DLL with M inverter stagers, first order filter.
- Lock time on the order of  $10\ \mu\text{s}$ . With digital, amortized calibration time **should** be much lower than this.
- With first order loop filter,  $9.9 \cdot \tau$  is required for  $\pm 50$  ppm settling.
  - For  $10\ \mu\text{s}$  settling time, given
$$t_{\text{settled}} = 9.2 / (2\pi f_p) \rightarrow f_p = 157\ \text{kHz}.$$
- with  $2^N = M$  stages, tap stages  $M/2$  ( $\bar{I}$ ),  $3M/4$  ( $\bar{Q}$ ) and  $M$  ( $I$ ) to use simple IQ based charge pump/phase detector circuit on the right.



# Digital TDC

## Calibrated Delay line

 

- Standard M-stage inverter-based delay line.
- Use mux to allow for delay line to operate as ring oscillator
- Measure phase with TDC of free-running oscillator.
  - Change in phase between measurements is related to error of the delay line.
- If  $\Delta t_{line}$  is the delay error of the delay line:

$$\frac{\Delta t_{line}}{T_{ref}} = \frac{\Delta TDC(N_{CYCLES})}{M \cdot N_{CYCLES}} \quad (7)$$


# Digital TDC - Algorithm

## Calibrated Delay line

- For  $\pm 50$  ppm accuracy, 10% tuning range and 10-bit DAC is sufficient.
- Use binary search algorithm to find optimal tuning word.
  - Frequency measurement granularity increases with measurement period, start coarse and increase double time with step of binary search
- With  $M=64$ , and 10 bits, search will take  $128 \mu\text{s}$ .
- (May also require some coarse calibration, this is expected to be fast)
- Better than analog if we calibrate less than 1 in 13 power ups.
  - 40 power-ups a second with 10 sec between calibrations this is amortizes to  $0.32 \mu\text{s}$  calibration time per wake up.

# Digital TDC

## Counter-based TDC

 

- Use synchronous counter clocked by oscillator to keep track of phase.
- Loop filter samples the counter phase every reference clock cycle.
- **Requires no calibration.** Linearity good.
- Resolution is  $\log_2(2.4G/16M) = 7.2$  bits. Good enough.
- Instant start up.
- **Power will be an issue???**
- Will have to test in simulation...

# DCO frequency tuning and $K_{DCO}$

## Resolving unknowns

- The fractional tuning range of the oscillator is:

$$\frac{\Delta f}{f_c} = \frac{1}{2} \cdot \frac{\gamma V_{DD} (1 - \ln 2)}{V_{DD} \left( \frac{7}{8} - \ln 2 + \frac{\gamma}{2} - \frac{\gamma}{2} \ln 2 \right) - V_{t0} (1 - \ln 2)} \quad (8)$$

- If a N-bit DAC is used to control the oscillator, the resulting DCO gain is therefore:

$$K_{DCO} = \frac{\Delta f}{2^{N_{DAC}}} = \frac{f_c}{2^{N_{DAC}+1}} \cdot \frac{\gamma V_{DD} (1 - \ln 2)}{V_{DD} \left( \frac{7}{8} - \ln 2 + \frac{\gamma}{2} - \frac{\gamma}{2} \ln 2 \right) - V_{t0} (1 - \ln 2)} \quad (9)$$

- The variation of the DCO gain, given the parameters it depends on is:

$$\sigma_{K_{DCO}} = \sqrt{\left( \frac{\partial K_{DCO}}{\partial V_{DD}} \cdot \frac{\sigma_{V_{DD}}}{K_{DCO}} \right)^2 + \left( \frac{\partial K_{DCO}}{\partial V_{t0}} \cdot \frac{\sigma_{V_{t0}}}{K_{DCO}} \right)^2 + \left( \frac{\partial K_{DCO}}{\partial \gamma} \cdot \frac{\sigma_{\gamma}}{K_{DCO}} \right)^2} \quad (10)$$

- For example: 1% variation in all parameters yields ca. 6% variation in tuning.

# DCO fix


## Updating phase noise model

- Fixed phase noise model in time domain simulation of PLL.
- Before phase noise was not accurately set, just loosely.
- Derived a Z-domain model for discrete random phase walk, am able now to convert continuous time phase noise spec to a discrete time model with accurate phase noise.


# Loop Filter Change

## Change to PID based loop filter

- **Old:** Complicated.

 

 
- **New:** Much simpler PID-based, added phase accumulator to handle wrap-over issues, allows for more stable control. Calibration should prevent accumulator overflow. Derivative path only used for calibration (not shown).





# Loop Filter

## Coarse frequency offset estimation

 

- **Coarse frequency estimation:** Given M-step TDC, outputting phase error signal  $e_\phi[n]$ , and a divider modulus N

$$\Delta \phi_{DCO}[n; q] = N \cdot \Delta \phi_{REF}[n] = 2\pi \frac{N}{M} (e_\phi[n] - e_\phi[n - q]), \quad \Delta \phi_{DCO}[n; q] = \Delta \omega_{DCO}[n] q T_{ref} = 2\pi q \frac{\Delta \tilde{f}_{DCO}}{f_{ref}} \quad (11)$$

$$\Delta \tilde{f}_c = \Delta \tilde{f}_{DCO} = \frac{f_{ref}}{q} \frac{N}{M} (e_\phi[n] - e_\phi[n - q]) \quad (12)$$

- Is a discrete differentiator, with gain coefficient to convert  $d\phi/dt$  to frequency.
  - Design logic to handle phase wrapping.
  - Useful in coarse frequency range calibration. Can detect fast if frequency offset too large.
  - Delay  $q$  is used to increase frequency resolution.

# Frequency Calibration (New)

## Coarse frequency calibration algorithm

- Use binary search algorithm to tune capacitor bank for frequency range.
- With 75 cycles measurement time, 2.4 GHz RF frequency, 16 MHz reference, and 64 TDC steps, within 0.5 MHz can be measured in 5  $\mu$ s
- A 4 bit binary search would take circa 20  $\mu$ s to execute.
- Should hopefully put initial frequency of PLL in lock range, and avoid issues with phase wrapping in the phase error accumulator.

# Specification (changed)

## System Performance Targets

Parameter	Value	Unit	Notes
Frequency	2.4-2.4835	GHz	2.4G ISM Band
Ref. frequency	16	MHz	Yields 6 channels
Power	$\leq 100$	$\mu\text{W}$	
Residual FM	$\leq 107$	$\text{kHz}_{\text{RMS}}$	$\text{BER} \leq 1\text{e-}2$ , $f_{\text{dev}} = \pm 250 \text{ KHz}$
Initial Lock Time	$\leq 50$	$\mu\text{s}$	Upon cold start
Re-lock Time	$\leq 5$	$\mu\text{s}$	Coming out of standby
Bandwidth	<del>100</del> 50	<del>kHz</del>	(nominally), tunable

Additionally: PLL output should support IQ sampling at LO frequency.


# Specification (changed)

## PLL Component Performance Targets

Parameter	Value	Unit	Notes
DCO LSB Resolution	$\leq 50$	kHz	Determined from quantization noise.
DCO DNL	$< 1$	LSB	Ensures monotonicity
TDC Resolution	<del>3.8</del> 0.95	ns	
TDC Resolution (bits)	<del>4.03</del> 6	bits	

# Architecture (unchanged)

## Block Diagram

 

## Power Targets

DCO	TDC	Divider	Other	SUM
70 $\mu$ W	20 $\mu$ W	10 $\mu$ W	$\ll 1$ $\mu$ W	100 $\mu$ W

# Project Phases

## Autumn 2019

- System modeling and simulation.
  - Learn PLL theory in detail
  - Evaluate feasibility of PLL architectures (counter, TDC-based)
  - Determine requirements for TDC/DCO/Divider/logic (bits of resolution, accuracy etc) to meet PLL performance specifications.
  - Determine digital logic for loop filter, validate stability and lock time performance.
- Research ultra-low power circuit topologies to implement system components that will meet determined requirements.
- Translate component-level specifications into schematic-level circuit designs.
  - Try, fail, try again until functional at schematic level.
    - I expect the TDC to be difficult.

# Project Phases (continued)

## Spring 2020

- Finalize schematic-level design.
- Establish thorough tests for PLL performance (automated?) to help in layout.
- Layout of PLL.
  - Design iteration until design specs met.
  - Probably very time consuming.
- Full characterization/validation of design performance.
  - Comprehensive Corners/Monte-Carlo testing (time consuming??)
  - More design iteration if new issues crop up...
- Thesis paper writing.