

# **Ultra-Low Power PLL for Wake-up Receiver Applications**

**Specialization Project Progress - 7th Week**

Cole Nielsen

Department of Electronic Systems, NTNU

11 October 2019 (Calendar week 41)

# Autumn Timeline

Week	Dates	Tasks	Outcomes
36	2.9 - 8.9	Review PLL Design	Refreshed Knowledge
37	9.9 - 15.9	Modeling/simulation (set up)	–
38	16.9 - 22.9	Modeling/simulation	TDC/DCO Requirements
39	23.9 - 29.9	Modeling/simulation	Loop Filter/Digital Algorithms
40	30.9 - 6.10	Modeling/simulation	Loop filter, DCO, TDC, calibration
41	7.10 - 13.10	Circuit Research	DCO/Divider topologies, Ideal Virtuoso implementation
42	14.10 - 20.10	Circuit Research	TDC/other topologies
43	21.10 - 27.10	Circuit Implementation	Digital logic (schematic)
44	28.10 - 3.11	Circuit Implementation	DCO (schematic)
45	4.11 - 10.11	Circuit Implementation	Divider/other (schematic)
46	11.11 - 17.11	Circuit Implementation (TDC)	
47	18.11 - 24.11	Circuit Implementation (TDC)	TDC (schematic)
48	25.11 - 1.12	Full Circuit testing	Testbenches, find bugs, design fixes
49	2.12 - 8.12	Full Circuit testing	Design Fixes/iteration
50	9.12 - 15.12	–	–

Legend: Done Current Revised

# Timeline Tasks

## This week

### — Simulation of PLL


- Finalized design of loop filter.
- Made script to compute filter coefficients for difference equation.
- Made new Python PLL simulation, completely in phase domain.
- Wrote Verilog module that implements loop filter.
- Working on schematic-based implementation of ideal PLL in Virtuoso...

### — DCO/Divider topologies:

- Considered LC versus ring oscillator.
  - Power limitations
  - Start up time, tuning
- Divider topologies
  - Synchronous counter (replaces divider and TDC)
  - $2^N$  to  $2^{N-1}$  multimodulus with N chained 2/3 dual-modulus dividers.
  - TSPC FF's to save power.

# PLL Simulation

## Final loop filter

 


- Proportional-integral with added pole. Equal to second order type-2 (i.e. charge pump) PLL. (PI is chosen for no tracking error).
- Additional pole yields more favorable oscillator and TDC noise characteristics.
- **Not** second order, really three poles and one zero (open loop  $A(f)$  shown below).
  - Computationally optimize loop filter transfer function so closed loop response approximates desired second order transfer function.

$$A(s) = \frac{K}{s^2} \cdot \frac{(s/\omega_z + 1)}{(s/\omega_p + 1)} \quad (1)$$

# PLL Simulation

## Computation of discrete filter.

 


- **Goal:** Convert prototype second order response as defined by  $\omega_n, \zeta$  and translate to a difference equation implementable in digital logic.
- PLL closed loop response  $G(s)$  is fit to the prototype response using gradient descent optimization of the parameters of  $A(s)$ :
  - PLL open loop response  $A(s)$  is computed from  $G(s)$ . The loop filter response  $h(s)$  is computed from  $A(s)$
  - $h(f)$  is discretized as  $h(z)$ ,  $h(z)$  is translated into a difference equation  $y[n]$ .
  - Difference equation is implemented as multipliers, adders and registers.

$$G(s) = \frac{A(s)}{1 + A(s)}, \quad A(s) = \frac{M}{N} \frac{K_{DCO}}{s} h(s), \quad h(s) = \frac{k_i}{s} \frac{s/\omega_z + 1}{s/\omega_p + 1}, \quad \omega_z = \frac{k_i}{k_p} \quad (2)$$


# PLL Simulation

## Discrete time implementation.

Continuous time filter

 

Discrete time filter

 

$$y[n] = x[n] \frac{K_i \omega_p T}{\omega_z} \frac{1 + \omega_z T}{1 + \omega_p T} - x[n-1] \frac{K_i \omega_p T}{\omega_z} \frac{1}{1 + \omega_p T} + y[n-1] \frac{2 + \omega_p T}{1 + \omega_p T} - y[n-2] \frac{1}{1 + \omega_p T}$$

$$= a_0 x[n] + a_1 x[n-1] - b_1 y[n-1] - b_2 x[n-2] \quad (3)$$




— Implementation requires:

- **3 registers** (delay elements)
- **4 multipliers**
- **3 adders**

# PLL Simulation
   
## Example filter.


- Using the described method, a filter was fitted to a 50 kHz bandwidth and  $\zeta \approx 0.7$ , for a 2.4 GHz PLL with 16 MHz reference and 64 TDC steps.
- Fitted response is close to prototype, but with a benefit:
  - DCO noise is attenuated by 40 dB/decade below loop bandwidth (versus 20 for prototype filter)



# PLL Simulation
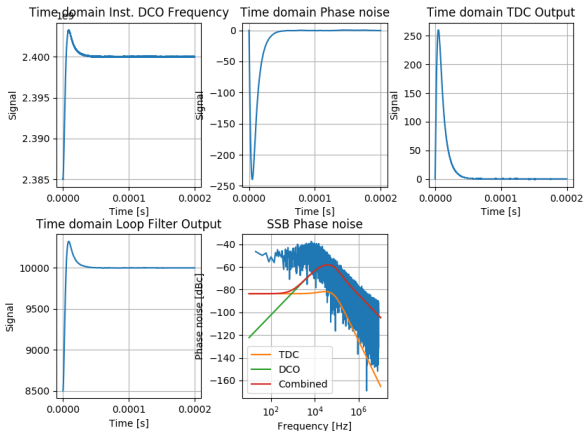
## Python simulation results.


- Modified Python simulation to be 100% phase domain, for better phase noise resolution.
- Loop filter design successful - architecture achieves lock and rejects phase noise.
- There is a error in my filter design math/code, PLL bandwidth in simulation is 5x smaller than intended.





# PLL Simulation

## Loop filter Logic Implementation.

 

- Translation to hardware:
  - Delay blocks are implemented as registers (3 total)
  - Gain blocks are implemented as multipliers (4 total)
  - Sums are adders (3 total)
- Decide bits of resolution for datapath on TDC/DCO resolution and gain coefficients.
- Will re-evaluate resolution based on power consumption after synthesis/place+route.

# PLL Simulation

## Resolution of datapath.

- Will use signed integers representing fixed point values.
- TDC resolution ( $N_{TDC}$ ) defines required number of integer bits on input.
- DCO resolution ( $N_{DCO}$ ) defines required number of integer bits on output.
- Fractional bits needed is (for gains, but applied to all):

$$\text{Fractional bits} > \lceil -\log_2(a_0 + a_1) \rceil \quad (4)$$

- Integer bits needed for gain coefficients:

$$\text{Integer bits} > \lceil 1 - \log_2(\max(|\{a_0, a_1, b_1, b_0\}|)) \rceil \quad (5)$$

- It is expected that the minimum *required* resolutions will then be:
  - Input : 6 integer bits, 0 fractional
  - Gains : 2 integer bits, 9 fractional
  - Output : 10 integer bits, 0 fractional
- (The filter coefficients  $a_0, a_1, b_1, b_0$  are on the order of 1)

# PLL Simulation

## Verilog implementation.


- Currently more bits than needed. Will make more efficient implementation later.
- Use fixed point with 4 integer bits + 12 fractional bits for filter coefficients.
- Input and output are 16 bit signed integers.
- Will multiplication/addition here be handled in synthesis, or do I need to do this?

```
1 module loop_filter
2 (
3     // filter coefficients have 4 integer bits and 12 fractional
4     input signed [15:0] xin,
5     input signed [15:0] a0, a1, b1, b2, yinit,
6     input clock, arst,
7     output signed [15:0] yout
8 );
9
10 reg signed [15:0] x1_reg;
11 reg signed [31:0] y1_reg, y2_reg; // 16 fractional 16 integer
12 wire signed [31:0] y0;
13 wire signed [32:0] axsum;
14 wire signed [48:0] bysum;
15 wire signed [32:0] partial_bysun;
16 wire signed [33:0] sunsum;
17
18 assign axsum = a0*xin + a1*x1_reg;
19 assign bysum = b1*y1_reg + b2*y2_reg;
20 assign partial_bysun = bysum[48:16]; // reduce to 12 fractional bits
21 assign sunsum = axsum + partial_bysun;
22 assign y0[3:0] = 4'b0; // need to add 4 fractional bits
23 assign y0[30:4] = sunsum[26:0];
24 assign y0[31] = 1'b0;
25 assign yout = y1_reg;
26
27 always @ (posedge clock or posedge arst) begin
28     if (arst) begin
29         x1_reg <= {16{1'b0}};
30         y1_reg[31:16] <= yinit;
31         y1_reg[15:0] <= {16{1'b0}};
32         y2_reg[31:16] <= yinit;
33         y2_reg[15:0] <= {16{1'b0}};
34     end
35     else begin
36         x1_reg <= xin;
37         y1_reg <= y0;
38         y2_reg <= y1_reg;
39     end
40 end
41 endmodule
```

# PLL Simulation
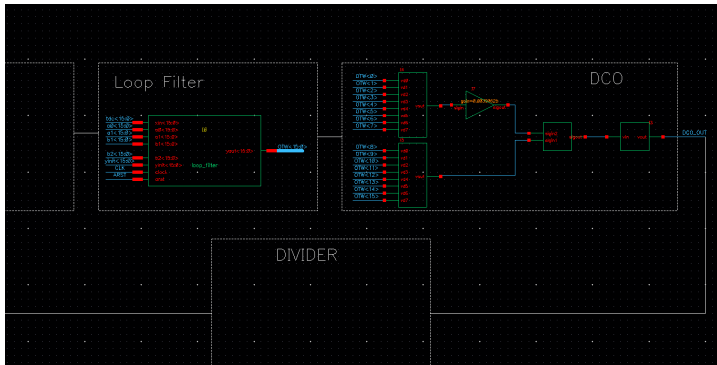
## Ideal PLL - Virtuoso schematic.

- Have loop filter (imported from Verilog module) and DCO implemented.
- Need to implement divider/TDC in Verilog (couldn't be easily done with ahdlLib).
  - Wasted quite a bit of time re-learning Verilog, so ran out of time for this.




# DCO topologies

## LC Oscillator versus Ring Oscillator.


### — LC Oscillator.

- Inductor Q and  $g_m/I_D$  doesn't scale well with process.
- Thus minimum  $I_D$  for  $A_V = g_m R_p > 1$  needed for startup doesn't scale well.
- At 2 GHz, need  $>60\mu W$  minimum to satisfy start-up conditions. Power increased by extra phases and margin needed to account for variation.
- Start-up time  $\gg 1\mu s$ .
- Requires level control, buffering to drive mixers.
- **Good phase noise.**

 **2 GHz oscillator minimum power versus process node scaling analysis from pg. 89 of [1].**



 (a) LC oscillator and ring oscillator schematics



(b) Simulated power consumption

# DCO topologies


## LC Oscillator versus Ring Oscillator.

### — Ring oscillator

- Ring oscillator power scales well with process node. In 20 nm can achieve 2 GHz oscillator with ca.  $1\mu W$
- Extra phases with little to no power penalty.
- Instant start-up.
- Can reset to known phase, which can be exploited in PLL for faster lock.
- Small area.
- **Bad phase noise (+20 dB vs LC).**

— **Conclusion:** LC power prohibitive, have to use ring oscillator.

Oscillator figure of merit comparison.

 


# DCO topologies

## Ring oscillator architecture.

- Proposed ring oscillator:  
pseudo-differential with back-gate control of frequency.
- Frequency tuning is highly linear with  $V_{ctrl}$ , allows for  $0-V_{DD}$  control range.
- Use DAC to set control voltage (10 bit?) for medium frequency tuning.
- Design for 10% fractional tuning range, so 10 bits is 240 kHz/LSB at 2.4 GHz.
- Utilize 5-bit unit-capacitor based digital capacitor for fine tuning, approximately 7.5 kHz/LSB
- Need frequency step to be  $\ll$  PLL bandwidth (50 kHz).

 **Pseudo-differential ring oscillator utilizing backgate-based coupling and frequency control.**



# DCO frequency tuning and $K_{DCO}$

## Backgate coupled pseudo-differential ring oscillator

- The center frequency of the oscillator, with  $V_{ctrl} = V_{DD}/2$ :

$$f_c = \frac{\mu_n C_{ox}}{4 \ln 2 N C} \left( \frac{W}{L} \right)_n \left[ V_{DD} \left( \frac{7}{8 \ln 2} - 1 + \frac{\gamma}{2 \ln 2} - \frac{\gamma}{2} \right) - V_{t0} \left( \frac{1}{\ln 2} - 1 \right) \right] \quad (6)$$

- The fractional tuning range of the oscillator is:

$$\frac{\Delta f}{f_c} = \frac{1}{2} \cdot \frac{\gamma V_{DD} (1 - \ln 2)}{V_{DD} \left( \frac{7}{8} - \ln 2 + \frac{\gamma}{2} - \frac{\gamma}{2} \ln 2 \right) - V_{t0} (1 - \ln 2)} \quad (7)$$

- If a N-bit DAC is used to control the oscillator, the resulting DCO gain is therefore:


$$K_{DCO} = \frac{\Delta f}{2^{N_{DAC}}} = \frac{f_c}{2^{N_{DAC}+1}} \cdot \frac{\gamma V_{DD} (1 - \ln 2)}{V_{DD} \left( \frac{7}{8} - \ln 2 + \frac{\gamma}{2} - \frac{\gamma}{2} \ln 2 \right) - V_{t0} (1 - \ln 2)} \quad (8)$$



# Divider topologies
 
## Divider options.

- Divider design is more trivial than the other components.
- **Synchronous counter.**
  - Use ripple counter + TSPC FF's for low power.
  - Lower jitter due to being synchronous.
- **Multi-modulus divider (asynchronous).**
  - N chained 2/3 dual modulus dividers. 7 stage?
  - Tunable from  $2^N$  to  $2^{N+1} - 1$ . N = 7 yields 128-255 range for divider modulus.
- Jitter compounds with divider chains, effect on phase noise???



# Specification (unchanged)

## System Performance Targets

Parameter	Value	Unit	Notes
Frequency	2.4-2.4835	GHz	2.4G ISM Band
Ref. frequency	16	MHz	Yields 6 channels
Power	$\leq 100$	$\mu\text{W}$	
FSK BER	$\leq 1\text{e-}2$		2FSK with $f_{dev}=\pm 250\text{ KHz}$
Initial Lock Time	$\leq 50$	$\mu\text{s}$	Upon cold start
Re-lock Time	$\leq 5$	$\mu\text{s}$	Coming out of standby
Bandwidth	50	kHz	(nominally), tunable

Additionally: PLL output should support IQ sampling at LO frequency.


# Specification (unchanged)

## PLL Component Performance Targets

Parameter	Value	Unit	Notes
DCO LSB Resolution	$\leq 50$	kHz	Determined from quantization noise.
DCO DNL	$< 1$	LSB	Ensures monotonicity
TDC Resolution	0.95	ns	
TDC Resolution (bits)	6	bits	

# Architecture (unchanged)

## Block Diagram

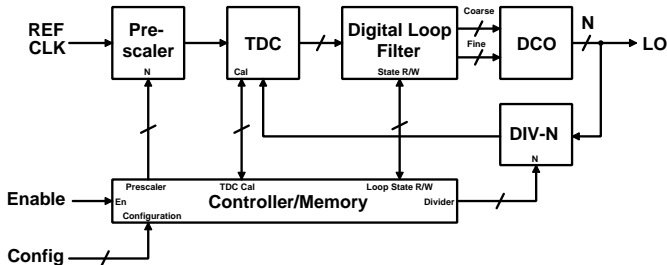

## Power Targets

DCO	TDC	Divider	Other	SUM
70 $\mu$ W	20 $\mu$ W	10 $\mu$ W	$\ll 1$ $\mu$ W	100 $\mu$ W

# Project Phases

## Autumn 2019

- System modeling and simulation.
  - Learn PLL theory in detail
  - Evaluate feasibility of PLL architectures (counter, TDC-based)
  - Determine requirements for TDC/DCO/Divider/logic (bits of resolution, accuracy etc) to meet PLL performance specifications.
  - Determine digital logic for loop filter, validate stability and lock time performance.
- Research ultra-low power circuit topologies to implement system components that will meet determined requirements.
- Translate component-level specifications into schematic-level circuit designs.
  - Try, fail, try again until functional at schematic level.
    - I expect the TDC to be difficult.

# Project Phases (continued)

## Spring 2020

- Finalize schematic-level design.
- Establish thorough tests for PLL performance (automated?) to help in layout.
- Layout of PLL.
  - Design iteration until design specs met.
  - Probably very time consuming.
- Full characterization/validation of design performance.
  - Comprehensive Corners/Monte-Carlo testing (time consuming??)
  - More design iteration if new issues crop up...
- Thesis paper writing.

# References

[1] "Ultra-Low Power Wake-Up Receivers for Wireless Sensor Networks", N. Pletcher, J.M Rabaey, 2008.

<http://www.eecs.berkeley.edu/Pubs/TechRpts/2008/EECS-2008-59.html>